



# Logic Circuit Design Lab (ICE2005)

Final Project

Instructor: Il Yong Chun, EEE & AI

(Revised by Il Yong Chun, 22-11-07)

# Agenda

---

- Computations in deep neural networks
- Project assignment






---

# Computations in Deep Neural Networks

# AI, ML, & DL...

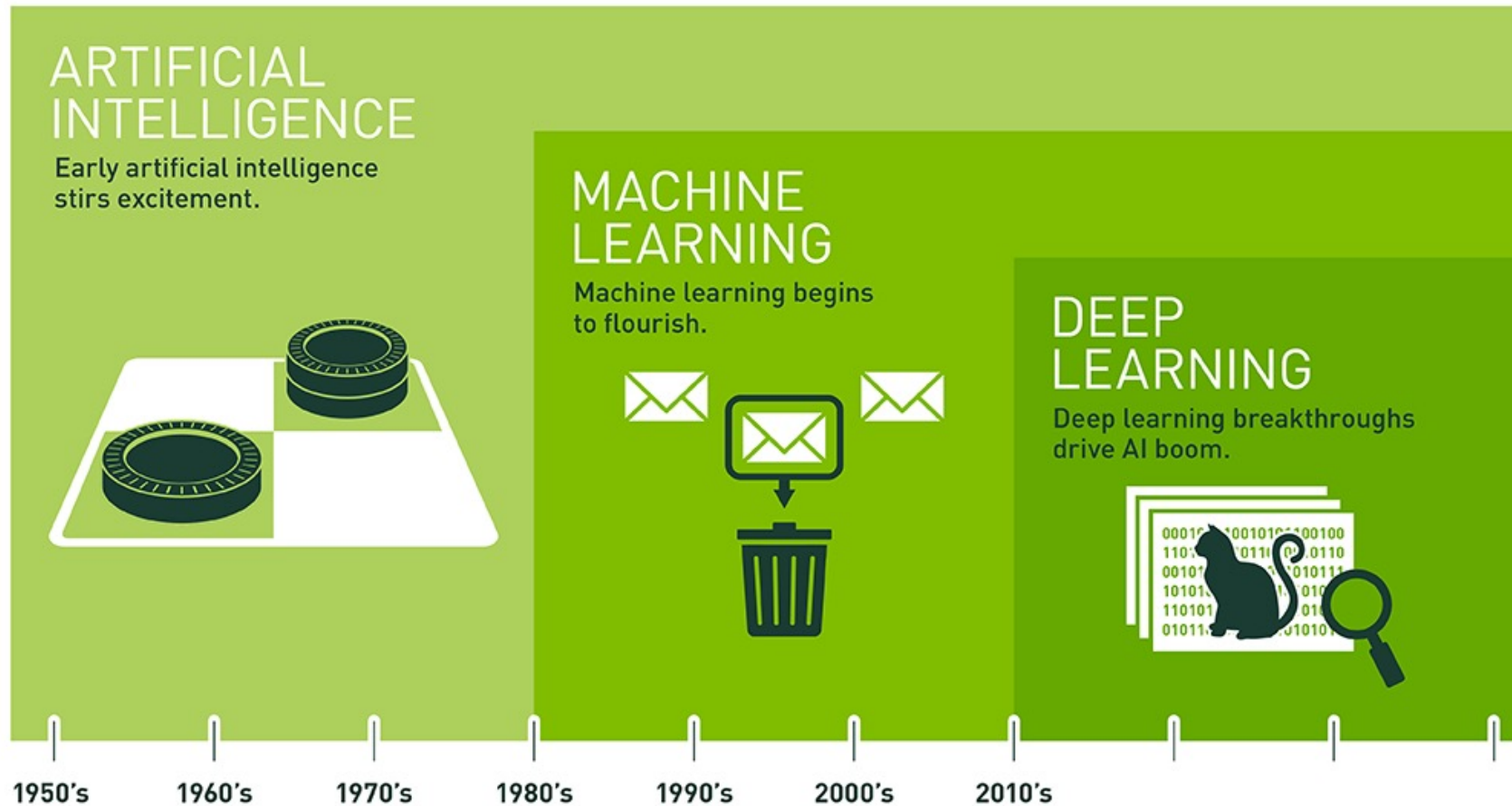

Since an early flush of optimism in the 1950s, smaller subsets of artificial intelligence – first machine learning, then deep learning, a subset of machine learning – have created ever larger disruptions.

\*Figure from NVIDIA  
(<https://developer.nvidia.com/deep-learning>)

# Deep Neural Networks (DNNs)

---




- Fully-connected networks (FCN)
- Convolutional neural network (CNN)
- Recurrent Neural Network
- Generative Adversarial Network
- Iterative Neural Network
- and more....




# DNN Example for Image Classification




- CNN+FCN

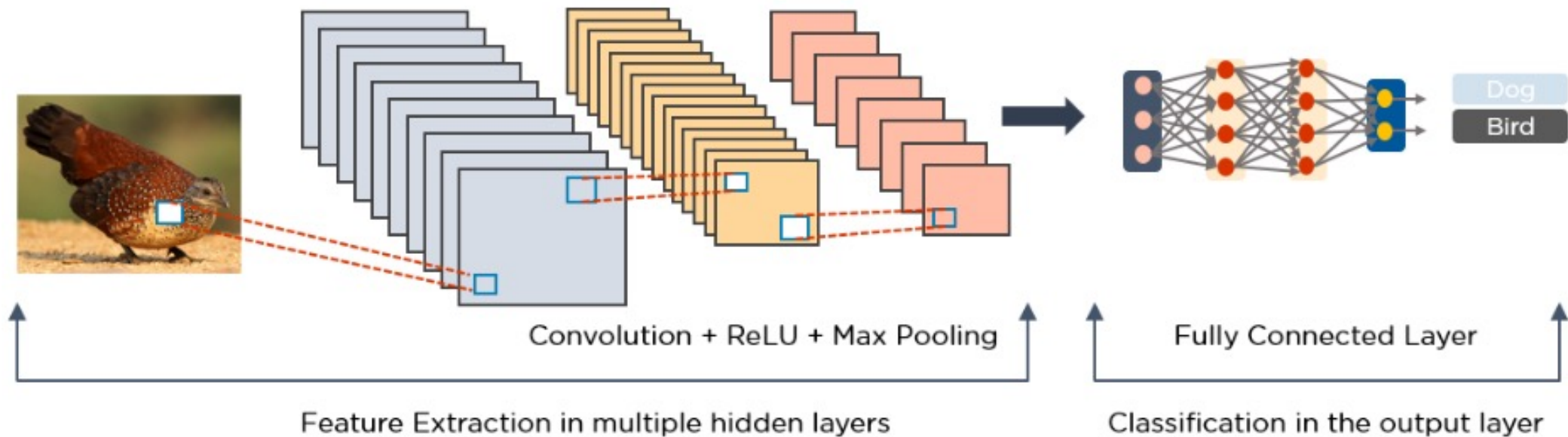

# DNN Accelerators

 

Google TPU

 

GPUs (including Tensor cores)

## What do they accelerate?

# Major Computations in DNNs




- 2D convolution: Aggregating sums of partial matrix multiplications

$A_{11}$	$A_{12}$	$A_{13}$	$A_{14}$
$A_{21}$	$A_{22}$	$A_{23}$	$A_{24}$
$A_{31}$	$A_{32}$	$A_{33}$	$A_{34}$
$A_{41}$	$A_{42}$	$A_{43}$	$A_{44}$

Input

$B_{11}$	$B_{12}$	$B_{13}$
$B_{21}$	$B_{22}$	$B_{23}$
$B_{31}$	$B_{32}$	$B_{33}$

Filter

 

$C_{11}$	$C_{12}$
$C_{21}$	$C_{22}$

Output

$$\begin{aligned} C_{11} = & A_{11} * B_{33} + A_{12} * B_{32} + A_{13} * B_{31} + \\ & A_{21} * B_{23} + A_{22} * B_{22} + A_{23} * B_{21} + \\ & A_{31} * B_{13} + A_{32} * B_{12} + A_{33} * B_{11} \end{aligned}$$

Rotated filter by 180 degree!

$B_{33}$	$B_{32}$	$B_{31}$
$B_{23}$	$B_{22}$	$B_{21}$
$B_{13}$	$B_{12}$	$B_{11}$



# Striding




$A_{11}$	$A_{12}$	$A_{13}$	$A_{14}$
$A_{21}$	$A_{22}$	$A_{23}$	$A_{24}$
$A_{31}$	$A_{32}$	$A_{33}$	$A_{34}$
$A_{41}$	$A_{42}$	$A_{43}$	$A_{44}$

Input

$B_{11}$	$B_{12}$	$B_{13}$
$B_{21}$	$B_{22}$	$B_{23}$
$B_{31}$	$B_{32}$	$B_{33}$

Filter

 

$C_{11}$	$C_{12}$
$C_{21}$	$C_{22}$

Output

What would the corresponding equation look like?

# Next Step




$A_{11}$	$A_{12}$	$A_{13}$	$A_{14}$
$A_{21}$	$A_{22}$	$A_{23}$	$A_{24}$
$A_{31}$	$A_{32}$	$A_{33}$	$A_{34}$
$A_{41}$	$A_{42}$	$A_{43}$	$A_{44}$

Input

$B_{11}$	$B_{12}$	$B_{13}$
$B_{21}$	$B_{22}$	$B_{23}$
$B_{31}$	$B_{32}$	$B_{33}$

Filter

 

$C_{11}$	$C_{12}$
$C_{21}$	$C_{22}$

Output

What would the corresponding equation look like?

# Last Step




$A_{11}$	$A_{12}$	$A_{13}$	$A_{14}$
$A_{21}$	$A_{22}$	$A_{23}$	$A_{24}$
$A_{31}$	$A_{32}$	$A_{33}$	$A_{34}$
$A_{41}$	$A_{42}$	$A_{43}$	$A_{44}$

Input

$B_{11}$	$B_{12}$	$B_{13}$
$B_{21}$	$B_{22}$	$B_{23}$
$B_{31}$	$B_{32}$	$B_{33}$

Filter

 

$C_{11}$	$C_{12}$
$C_{21}$	$C_{22}$

Output

What would the corresponding equation look like?




---

# Term Project
 
# Your Project

- A set of logic that computes a 2x2 output using
  - A single processing element (PE)
  - A 3x3 systolic array
  - A 2x2 systolic array
- Do the following.
  - Simulation study
  - Verifying your design by displaying results.





# Design Overview (1/2)




- **Controller**

- Initializes and of memory, computation module, and display module.
- Takes controls of all the modules.
- For each module, if you need a micro-control inside it, you can implement that control flow in the corresponding module.

- **Memory** keeps and outputs the numbers of

 - An input matrix (16 numbers)
- A filter (9 numbers)




SA: Systolic Array
 
# Design Overview (2/2)




- **Computation module** performs computations in two modes.
  - **Serial mode**: Compute with a single PE.
  - **Parallel mode 1**: Compute with 3x3 systolic array.
  - **Parallel mode 2**: Compute with 2x2 systolic array.
- **Display module** shows computation results.



SA: Systolic Array

# Execution Flow

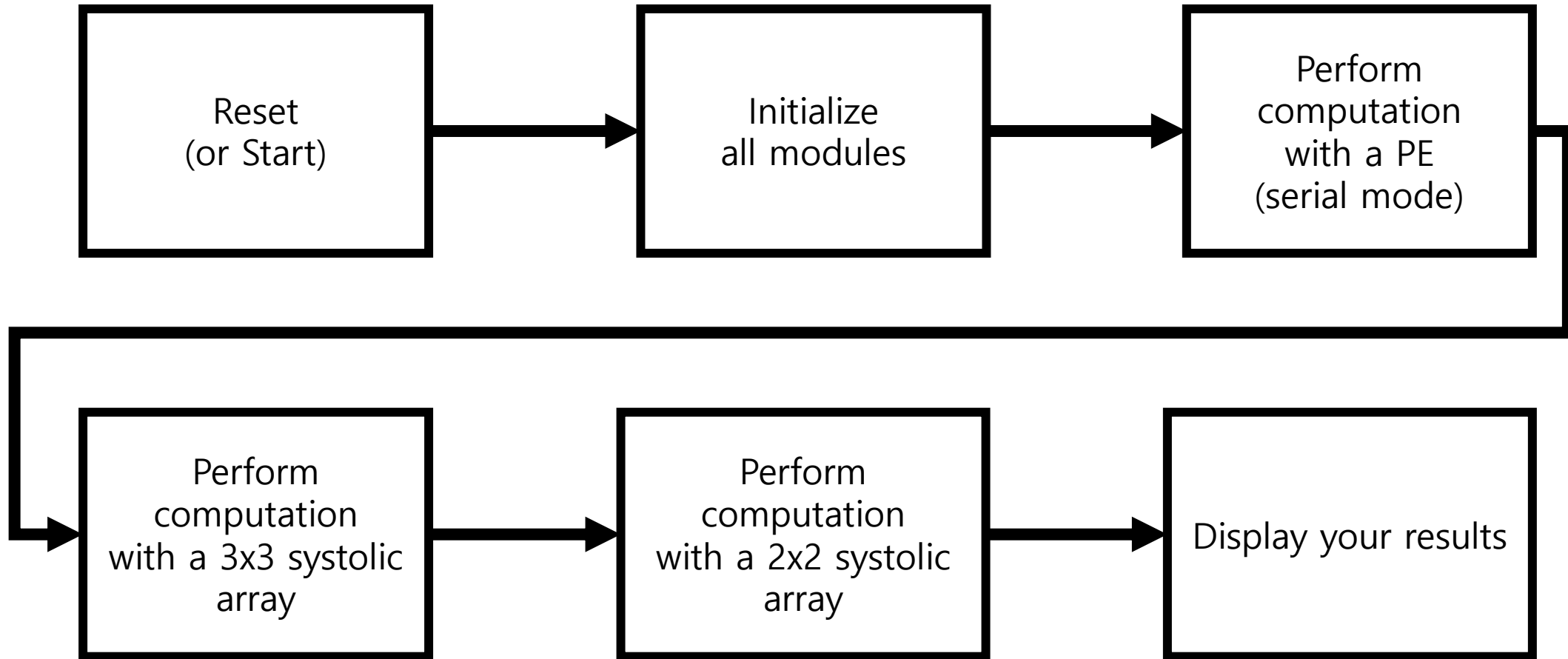

# Simulation Study (1/3)

---




- Set a test plan for each module (7 testbench files)
  - Controller
  - Memory
  - PE
  - Two systolic arrays
  - Display module
  - Top module
 
# Simulation Study (2/3)



- Do performance comparisons
  - A single PE vs a systolic array



$$X = \text{Speedup}_{BA} = \frac{\text{Execution Time}_A}{\text{Execution Time}_B}$$



# Simulation Study (3/3)

---



- Report the following
  - Speedup of 3x3 systolic array over a single PE
  - Speedup of 2x2 systolic array over a single PE

# Verification

---



- Show all the computation results.
  - 4 values in 2x2 output matrix
    - Computed by a 3x3 systolic array
    - Computed by a 2x2 systolic array
    - More details in Requirement 5
  - `$display` or any other visualization method is fine.
    - Make sure to show each value of output and its corresponding index (e.g.,  $c_{\{1,1\}}$ ,  $c_{\{1,2\}}$ ).
- Don't need to display the results with a single PE.

# Requirement 0: General

---

- Follow the design overview.
- Follow the execution flow.
- Satisfy all the following requirements.
- Refer to the following implementation styles.
- Everything except the execution flow and the guidelines are free to choose/design/implement.

**Remind that you may follow the honor code.**

# Requirement 0: General (2/2)

---




- All the numbers in the input matrix, the filter, and the output (output matrix) are 8-bit unsigned integers.
- If a calculation result incurs overflow, simply use the lower 8 bits only.
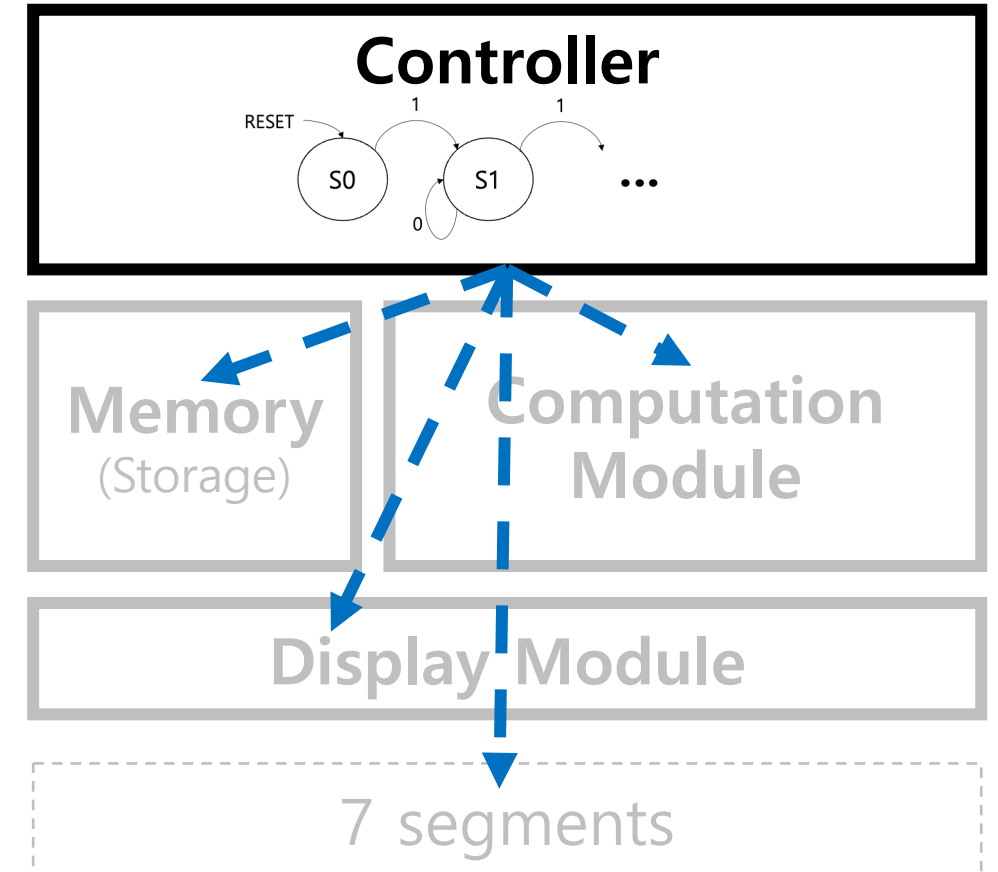
# Requirement 1: Controller



- Design your controller with state machine(s).  
**(Week 10)**
- Design a complete flow for initializing and taking controls of all the modules.  
(Memory, computation modules, and display modules)
- Moore machine or Mealy machine?  
→ Use what you prefer.
- Reset or Start: Design it as you want
  - You may use any buttons.
  - You may set an automatic reset or start.





 
# Requirement 2: Memory




- Implement it by yourself.
- **Memory** keeps and outputs the numbers of
  - An input matrix (16 numbers)
  - A filter (9 numbers)


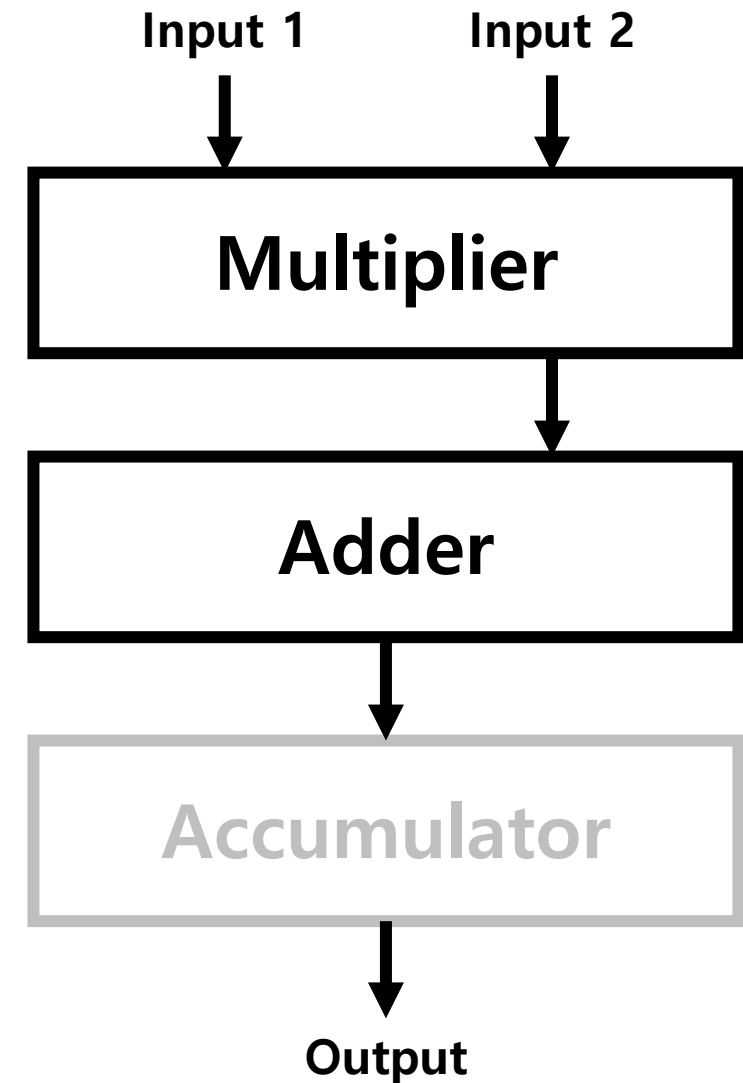
# Requirement 3: PE




- Three basic modules
  - Multiplier: You can implement it with adders.
  - Adder
  - Accumulator
    - It keeps an intermediate calculation result.
    - Decide the case that we need it.
    - If you don't need it at all, it's fine not to use it.
  - Any other resources?
- Implement the modules by reminding
  - Three modeling methodologies (**Week 2**)
  - Structural modeling (**Week 6**)
  - Adders with what? (**Week 3**)
  - Multipliers with what? (**Week 3**)
  - Registers with what? (**Week 8**)
- You may want to reuse your source codes implemented in previous labs.


 
# Requirement 4: Systolic Array (1/2)




- Implement a 3x3 systolic array.
- Implement the modules by structural modeling (**Week 6**).
- You may add any resources if needed.
  - Just, be clear about your design.
- Refer to an example. (Systolic\_Array\_Example.pdf)



 
# Requirement 4: Systolic Array (2/2)



- Implement a 2x2 systolic array.
- Implement the modules by structural modeling (**Week 6**).
- You may add any resources if needed.
  - Just, be clear about your design.
- Change the dataflow of the input matrix and the filter accordingly.
  - You should implement a different dataflow from the dataflow shown in "Systolic\_Array\_Example.pdf."



# Requirement 5: Display Flow

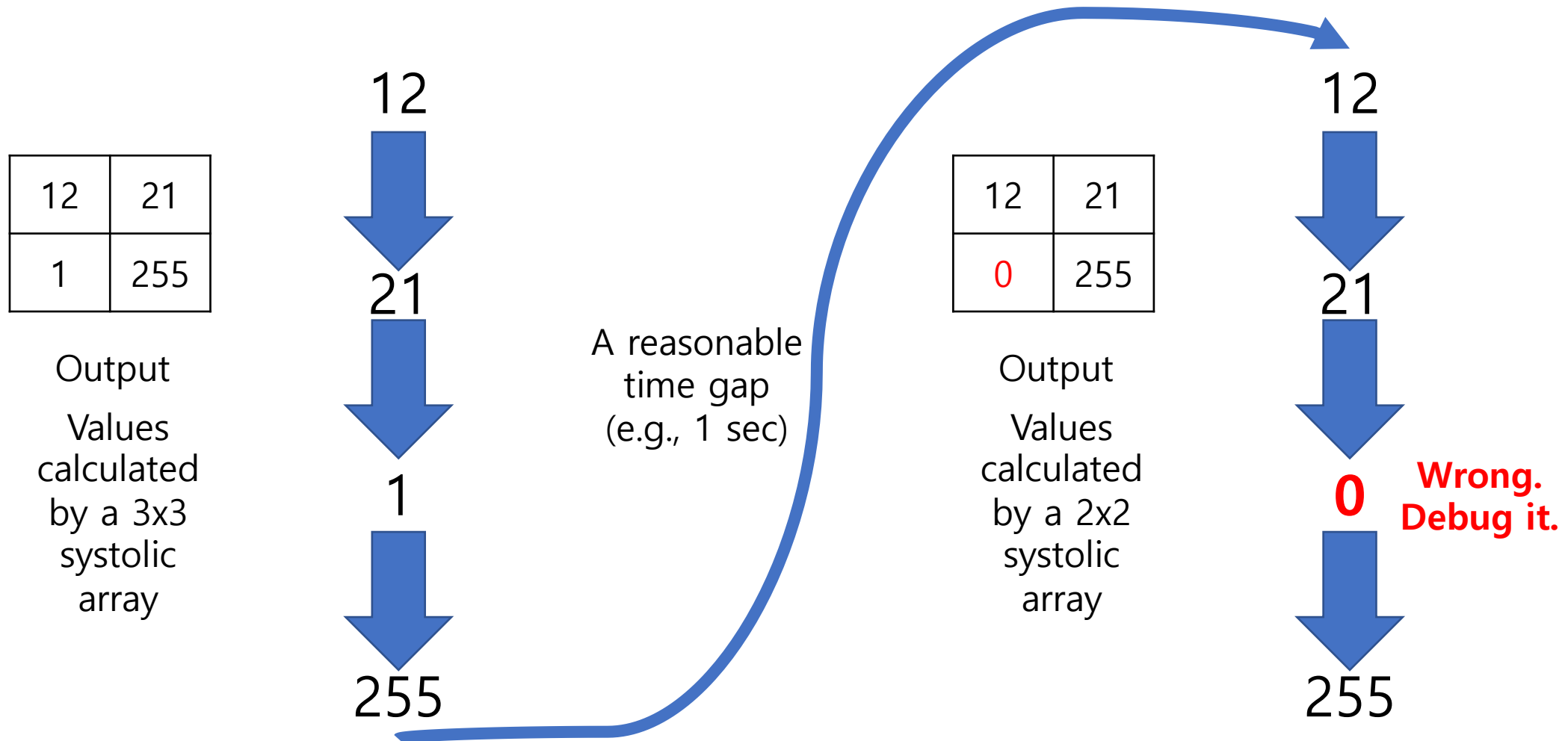



# Requirement 6: Demonstration


---



- Once you are done with implementing Requirements 1--5, let me or TAs know.
- We will give you a random 4x4 input matrix and a random 3x3 filter.
- Apply them to your source codes and show your calculation results following Requirement 5.
- If everything is ok, your demonstration is successful!
- Results from the final demo will be evaluated.
 
# Requirement 7: Top Module

- You may want to implement a top module.
- Top module
  - Includes all the modules.
  - does not include a test pattern.
  - Triggers initialization and makes your design work.
  - Interfaces with external components of your modules. (e.g., clock)
- Top module just activates all the modules and make them work.



# Requirement 8: Testbench

---



- Create a test bench file for each module.
- Report the simulation results, which you have been doing throughout this semester.
  - You may use ModelSim.

# Requirement 9: Collaboration

---



- Each member should implement at least one module and one testbench.
- All members review source code each other and make all the codes best.
- Have deep discussions regarding interfaces between the modules.
- Clearly write down what I emphasized above in your final report.

# Implementation Styles

---



- You would need structural modeling (**Week 6**) everywhere.
- Along with the structural modeling methodology, use either
  - Behavioral modeling: Easiest except for what?
  - Gate-level modeling: Hardest except for what?
  - If you use a more difficult methodology, I'll give a higher score.
  - Try to reuse the source code that you implemented during this semester.
- If you employ gate-level modeling, use
  - AND, OR, NOT gates that the instructor provided
  - XNOR gate
- For the controller, just use "behavioral modeling."

## Please find out what to do by yourselves.

- Remind that this is a project.
- Questions regarding the following will **never** be answered.
  - Specifications of the modules in this project  
ex) PE and systolic array structures, memory structure, etc.
  - Abstract questions  
ex) I can't compile. How can I fix it?

# Overall evaluation criterion

---



- **Simulation demonstration**

- Will be evaluated real-time in each class

- **Report**

- 1 report per group
- Page limit: 25 pages
- What to include
  - Brief description about the project's objective
  - Theoretical design (I believe that you all figure out what is needed.)
  - Simulation results and discussions (waveform, analysis, etc.)
  - Contributions from each team member.

- **Source code files**

# Share Your Questions

---



- Ask questions via
  - Q&A board in i-Campus (responses may be delayed)
  - Offline Q&A sessions
- Questions asked via any private channels, including
  - e-mails
  - i-Campus messages
  - phone calls**will *not* be answered.**



# Your Source Codes

---



- Upload to i-Campus
  - Copy all the files into the project folder.
  - Submit the zip file with your report to i-Campus.

# Deadline

---



- Refer to i-Campus.
- I STRONGLY recommend avoiding late submission.
- Each delay in submission of a second after the deadline will result in penalty in the attendance score.
- Each delay in submission of a day and more after the deadline will result in....
  - 0 score for the corresponding report.
  - **Regarded as an absence.**